

This is a help document for loop analysis method. As we know: There are three kinds of branches in distribution network. Constant PQ branches whose current is considered as knowns in the circuit analysis belong to *Set 2*. The other branches are voltage source branches belong to *Set 3*. The branch with constant impedance belong to *Set 1*

There are two kinds of loop, one loop is from PQ load to the voltage source belongs to *Set l1* There are two kinds of loop, one loop is not from PQ load to the voltage source belongs to *Set l2*

$$B_{l1,1}V_{b,1,re} + B_{l1,2}V_{b,2,re} + B_{l1,3}V_{b,3,re} = 0 \quad (1)$$

$$B_{l2,1}V_{b,1,re} + B_{l2,2}V_{b,2,re} + B_{l2,3}V_{b,3,re} = 0 \quad (2)$$

$$B_{l1,1}V_{b,1,im} + B_{l1,2}V_{b,2,im} + B_{l1,3}V_{b,3,im} = 0 \quad (3)$$

$$B_{l2,1}V_{b,1,im} + B_{l2,2}V_{b,2,im} + B_{l2,3}V_{b,3,im} = 0 \quad (4)$$

$$\begin{bmatrix} B_{l1,1} & B_{l1,2} \\ B_{l2,1} & B_{l2,2} \end{bmatrix} \begin{bmatrix} V_{b,1,re} \\ V_{b,2,re} \end{bmatrix} = \begin{bmatrix} -B_{l1,3}V_{b,3,re} \\ -B_{l2,3}V_{b,3,re} \end{bmatrix} \quad (5)$$

$$\begin{bmatrix} B_{l1,1} & B_{l1,2} \\ B_{l2,1} & B_{l2,2} \end{bmatrix} \begin{bmatrix} V_{b,1,im} \\ V_{b,2,im} \end{bmatrix} = \begin{bmatrix} -B_{l1,3}V_{b,3,im} \\ -B_{l2,3}V_{b,3,im} \end{bmatrix} \quad (6)$$

$$I_{b,1,re} = B_{l1,1}^T I_{l1,re} + B_{l2,1}^T I_{l2,re} \quad (7)$$

$$I_{b,1,im} = B_{l1,1}^T I_{l1,im} + B_{l2,1}^T I_{l2,im} \quad (8)$$

$$I_{b,2,re} = B_{l1,2}^T I_{l1,re} + B_{l2,2}^T I_{l2,re} \quad (9)$$

$$I_{b,2,im} = B_{l1,2}^T I_{l1,im} + B_{l2,2}^T I_{l2,im} \quad (10)$$

$$\begin{bmatrix} I_{b,1,re} \\ I_{b,2,re} \end{bmatrix} = \begin{bmatrix} B_{l1,1}^T & B_{l2,1}^T \\ B_{l1,2}^T & B_{l2,2}^T \end{bmatrix} \begin{bmatrix} I_{l1,re} \\ I_{l2,re} \end{bmatrix} \quad (11)$$

$$\begin{bmatrix} I_{b,1,im} \\ I_{b,2,im} \end{bmatrix} = \begin{bmatrix} B_{l1,1}^T & B_{l2,1}^T \\ B_{l1,2}^T & B_{l2,2}^T \end{bmatrix} \begin{bmatrix} I_{l1,im} \\ I_{l2,im} \end{bmatrix} \quad (12)$$

$$(r_b + jx_b)(I_{b,1,re} + jI_{b,1,im}) = V_{b,1,re} + jV_{b,1,im} \quad (13)$$

$$\begin{bmatrix} r_b & -x_b \\ x_b & r_b \end{bmatrix} \begin{bmatrix} I_{b,1,re} \\ I_{b,1,im} \end{bmatrix} = \begin{bmatrix} V_{b,1,re} \\ V_{b,1,im} \end{bmatrix} \quad (14)$$

We can derived that:

$$\begin{bmatrix} r_b & -x_b \\ x_b & r_b \end{bmatrix} \begin{bmatrix} B_{l1,1}^T I_{l1,re} + B_{l2,1}^T I_{l2,re} \\ B_{l1,1}^T I_{l1,im} + B_{l2,1}^T I_{l2,im} \end{bmatrix} = \begin{bmatrix} V_{b,1,re} \\ V_{b,1,im} \end{bmatrix} \quad (15)$$

both side multiplied by the equation:

$$\begin{bmatrix} B_{l2,1} & 0 \\ 0 & B_{l2,1} \end{bmatrix}$$

For PQ branch type 2, has no elements in $B_{l2,2}$, so $B_{l2,2} = 0$ $B_{l2,1}V_{b,1,re} + 0 + B_{l2,3}V_{b,3,re} = 0$.

$$\begin{bmatrix} B_{l2,1}r_b & -B_{l2,1}x_b \\ B_{l2,1}x_b & B_{l2,1}r_b \end{bmatrix} \begin{bmatrix} B_{l1,1}^T I_{l1,re} + B_{l2,1}^T I_{l2,re} \\ B_{l1,1}^T I_{l1,im} + B_{l2,1}^T I_{l2,im} \end{bmatrix} = \begin{bmatrix} B_{l2,1}V_{b,1,re} \\ B_{l2,1}V_{b,1,im} \end{bmatrix} \quad (16)$$

$$\begin{aligned} & B_{l2,1}r_b B_{l1,1}^T I_{l1,re} + B_{l2,1}r_b B_{l2,1}^T I_{l2,re} \\ & - B_{l2,1}x_b B_{l1,1}^T I_{l1,im} - B_{l2,1}x_b B_{l2,1}^T I_{l2,im} \\ & = -B_{l2,3}V_{b,3,re} \end{aligned} \quad (17)$$

$$\begin{aligned} & B_{l2,1}x_b B_{l1,1}^T I_{l1,re} + B_{l2,1}x_b B_{l2,1}^T I_{l2,re} \\ & + B_{l2,1}r_b B_{l1,1}^T I_{l1,im} + B_{l2,1}r_b B_{l2,1}^T I_{l2,im} \\ & = -B_{l2,3}V_{b,3,im} \end{aligned} \quad (18)$$

And then we can calculate the $I_{l1,re}, I_{l1,im}$ with $I_{l2,re}, I_{l2,im}$ as known.

$$\begin{aligned} & B_{l2,1}r_b B_{l2,1}^T I_{l2,re} - B_{l2,1}x_b B_{l2,1}^T I_{l2,im} \\ & = -B_{l2,3}V_{b,3,re} - B_{l2,1}r_b B_{l1,1}^T I_{l1,re} + B_{l2,1}x_b B_{l1,1}^T I_{l1,im} \end{aligned} \quad (19)$$

$$\begin{aligned} & B_{l2,1}x_b B_{l2,1}^T I_{l2,re} + B_{l2,1}r_b B_{l2,1}^T I_{l2,im} \\ & = -B_{l2,3}V_{b,3,im} - B_{l2,1}x_b B_{l1,1}^T I_{l1,re} - B_{l2,1}r_b B_{l1,1}^T I_{l1,im} \end{aligned} \quad (20)$$

Suppose that the branch direction of PQ load is from load point to the ground, Suppose that the voltage source direction is from ground to grid connected node.

$B_{l1,1}$ is path-branch matrix, the tree branch direction is from source node to load node.

loop 1 direction is from load point to ground. The matrix. $B_{l2,3}$ can be zero.

$B_{l2,1}$ should form according to the loop. the loop 2 direction is the same with the loop edge.